

# Electric Circuits & Electrical Safety

## Question Paper

Course	CIE IGCSE Physics
Section	4. Electricity & Magnetism
Topic	Electric Circuits & Electrical Safety
Difficulty	Medium


**Time Allowed**      **60**

**Score**                **/43**

**Percentage**        **/100**

### Question 1a

Fig. 10.1 shows an arrangement for making an electromagnet.

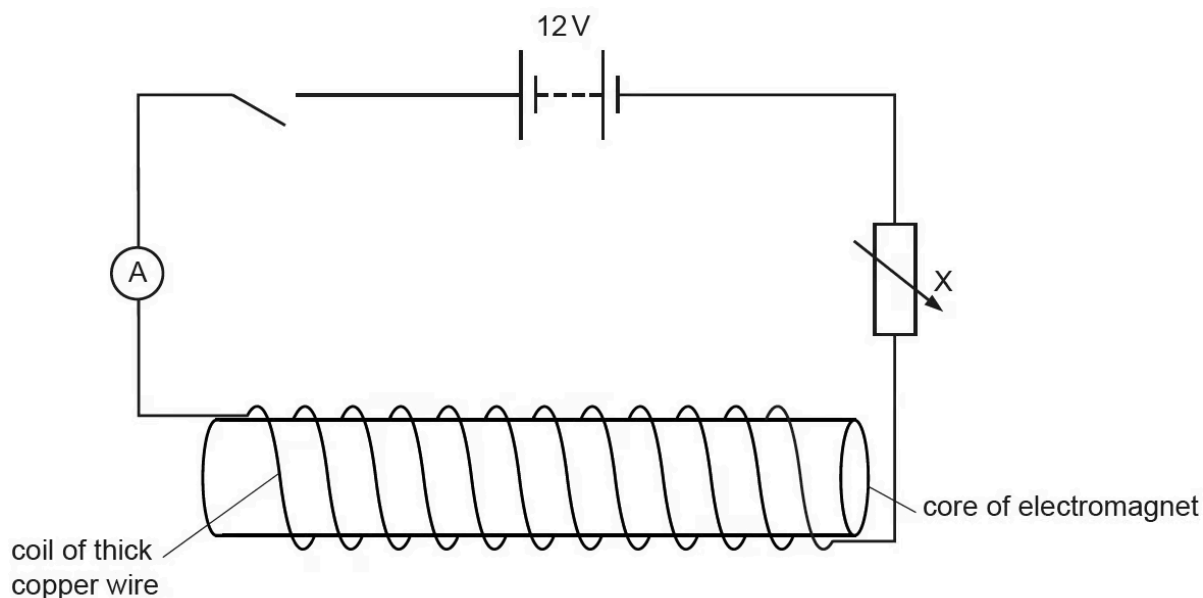

**Fig. 10.1**

- (i) State a material which is suitable for the core of the electromagnet. [1]
  
- (ii) State the name for component X in Fig. 10.1. [1]
  
- (iii) Describe and explain how component X varies the strength of the electromagnet. [2]

**[4 marks]**

**Question 1b**

The switch is closed. The reading on the ammeter is 1.5 A.


Calculate the resistance of the circuit.

resistance = .....  $\Omega$   
[3 marks]

## Question 2a

A student does an experiment to determine the resistance of a fixed resistor,  $R$ .

The student draws an incomplete diagram of the circuit, as shown in Fig. 10.1.

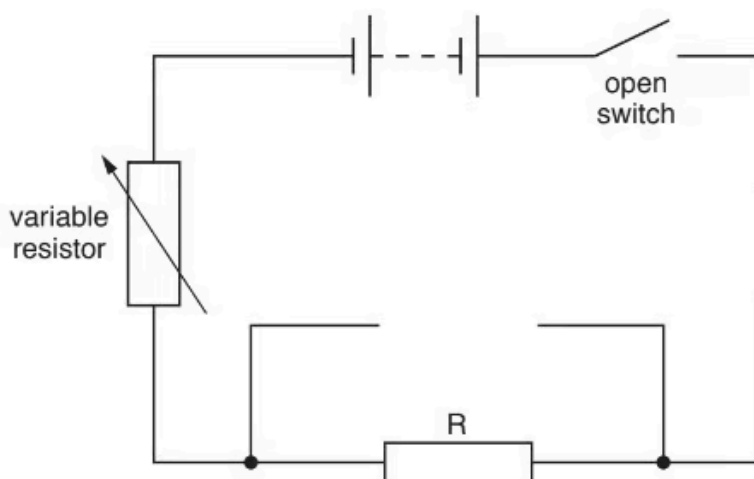


**Fig. 10.1**

- (i) On Fig. 10.1, draw the missing circuit symbols. [3]
- (ii) Describe how the student could use the circuit to determine a reliable value for the resistance of  $R$ . [5]

**[8 marks]**

**Question 2b**

Fig. 10.2 shows a  $20\ \Omega$  resistor connected to a power supply.

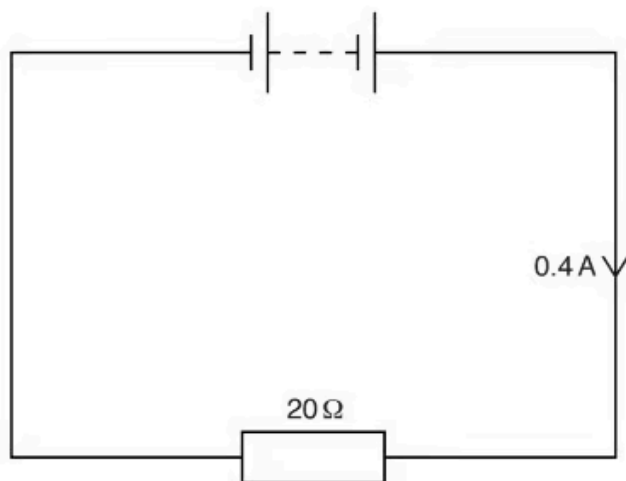

**Fig. 10.2**

A second  $20\ \Omega$  resistor is connected in series with the first.


State and explain how this affects the current in the circuit.

**[4 marks]**

### Question 3a

A teacher is investigating the resistance of a lamp.

Fig. 10.1 shows part of the circuit she uses. The circuit is incomplete.

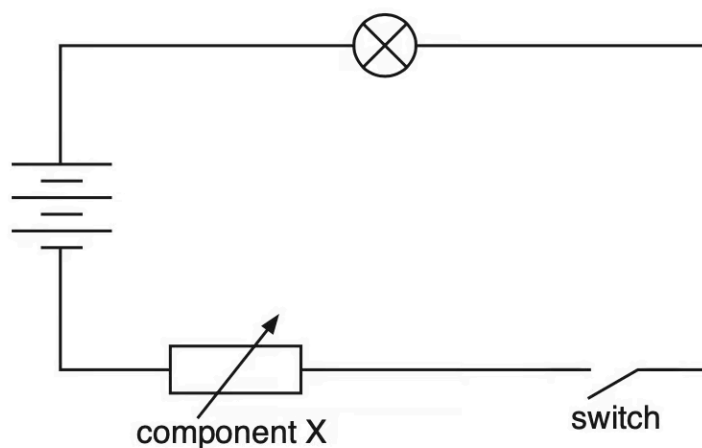

**Fig. 10.1**

- (i) To determine the resistance of the lamp, the teacher adds two meters to her circuit.

On Fig. 10.1, draw circuit symbols to show each meter correctly connected in the circuit.

[3]

- (ii) When the current in the lamp is  $0.25\text{ A}$ , the potential difference (p.d.) across the lamp is  $4.5\text{ V}$ . Calculate the resistance of the lamp.

resistance = .....  $\Omega$  [3]  
[6 marks]

### Question 3b

#### Extended tier only

- (i) State the name of component X. [1]
- (ii) Describe and explain how the teacher uses component X to investigate the resistance of the lamp. [2]
- [3 marks]

**Question 4a**

A teacher uses a power supply in a metal case. The circuit for the power supply includes a fuse.

- (i) Draw the electrical symbol for a fuse.

[1]

- (ii) The metal case of the power supply is earthed. A fault occurs and a live wire touches the metal case.

Explain how earthing the metal case protects the teacher.

[3]

**[4 marks]****Question 4b**

The power supply circuit includes a transformer. Its input voltage is 240 V. There are 960 turns on the input coil and 64 turns on the output coil.

Calculate the output voltage of the transformer.


output voltage = ..... V

**[3 marks]**



**Question 5a**

A circuit is made from two lamps, a cell and a switch, as shown in Fig. 10.1.

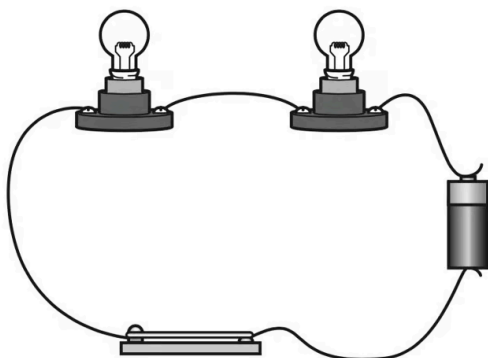

**Fig. 10.1**

- (i) Draw the circuit symbol for a cell. [1]
- (ii) State the term used for the arrangement of lamps in the circuit in Fig. 10.1. [1]
- (iii) The switch is closed and the lamps light.


State the name of the charged particles that are flowing through the wires.

[1]  
[3 marks]

## Question 5b

### Extended tier only

Fig. 10.2 represents a different type of circuit.

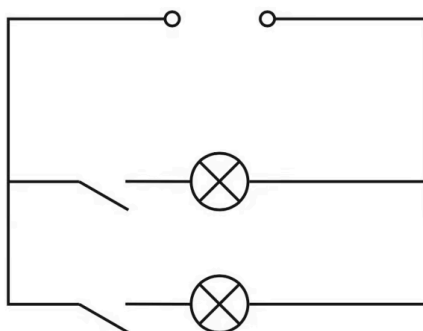

**Fig. 10.2**

- (i) Compare Fig. 10.1 and Fig. 10.2.  
State **two** advantages of the type of circuit shown in Fig. 10.2 with the type of circuit shown in Fig. 10.1. [2]
- (ii) The potential difference across the power source in Fig. 10.2 is 3.0 V. The combined resistance of the two lamps is 12  $\Omega$ .

Calculate the size of the current in the circuit when the switches are closed.

current = ..... A [3]  
[5 marks]



Head to [www.savemyexams.com](https://www.savemyexams.com) for more awesome resources