

Electric Circuits & Electrical Safety

Question Paper

Course	CIE IGCSE Physics
Section	4. Electricity & Magnetism
Topic	Electric Circuits & Electrical Safety
Difficulty	Medium

Time Allowed 40

Score /29

Percentage /100

Question 1

A student investigates a wind turbine, which is an electrical generator driven by a propeller blade.

Plan an experiment which will enable him to investigate how the current in a resistor connected across the terminals of the turbine varies with the speed of the air flow through the turbine.

The apparatus available includes:

- a model wind turbine as shown in Fig. 4.1
- an electric fan to provide the moving air to turn the turbine
- a device for measuring air speed.

In your plan, you should:

- list any additional apparatus needed
- complete the wind turbine circuit diagram on Fig. 4.1
- state the key variables to be kept constant
- explain briefly how to carry out the experiment, including how the speed of the air flow is to be changed
- explain how to use the readings to reach a conclusion.

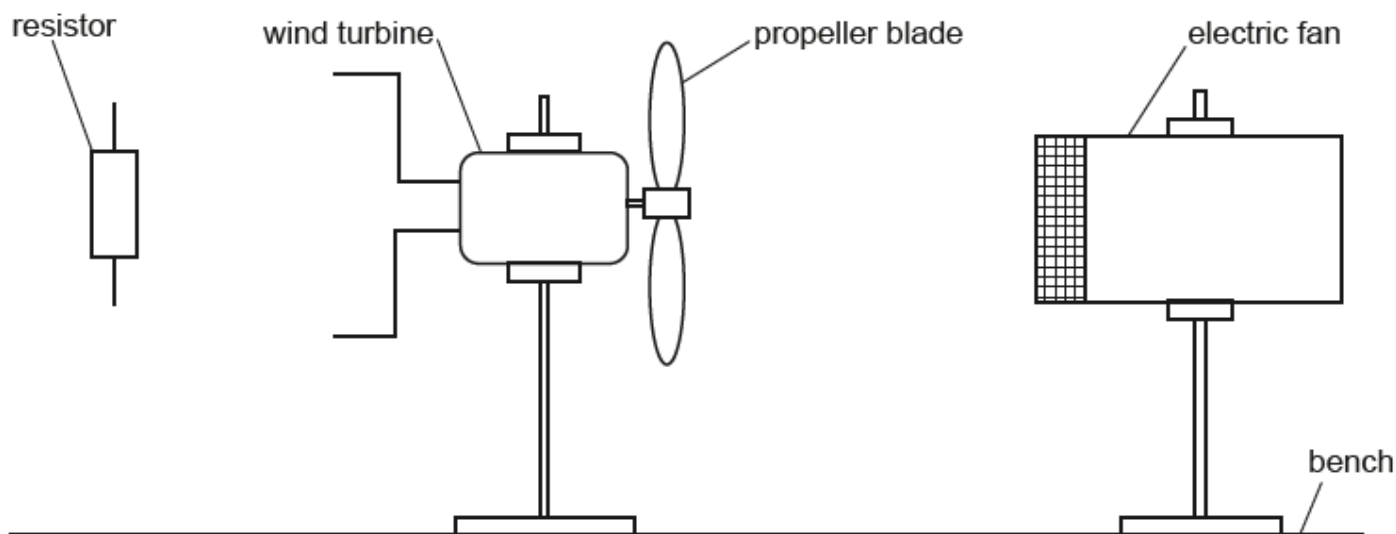


Fig. 4.1

[7 marks]

Question 2a

A student determines the resistances of some filament lamps.

Fig. 2.1 shows the first circuit she uses.

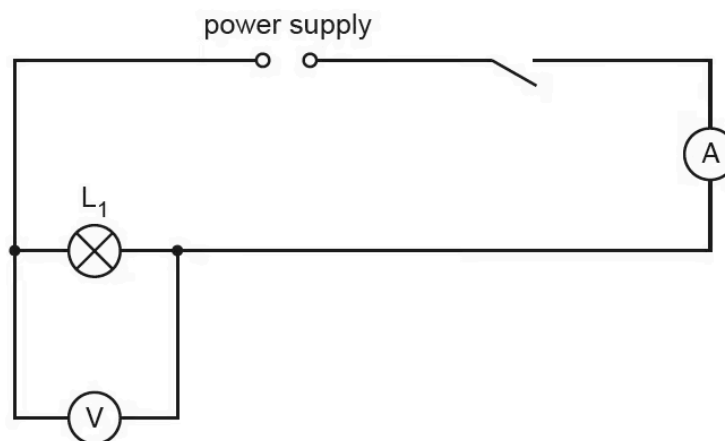


Fig. 2.1

- (i) Record the potential difference V_1 across the lamp L_1 , as shown on the voltmeter in Fig. 2.2.

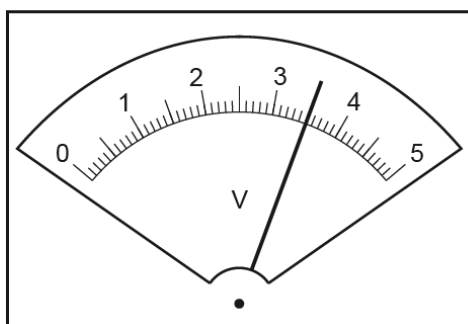


Fig. 2.2

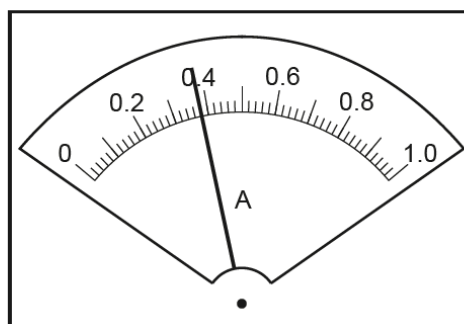


Fig. 2.3

$V_1 = \dots\dots\dots \text{ V [1]}$

- (ii) Record the current I_1 in the circuit, as shown in Fig. 2.3.

$$I_1 = \dots\dots\dots \text{A} \quad [1]$$

(iii)

Calculate the resistance R_1 of the filament of lamp L_1 . Use the equation $R_1 = \frac{V_1}{I_1}$. Include the unit.

$$R_1 = \dots\dots\dots [2]$$

[4 marks]

Question 2b

The student disconnects the voltmeter. She connects lamp L_2 in series with lamp L_1 . She connects the voltmeter across lamp L_2 .

She measures the current I_2 in the circuit and the potential difference V_2 across lamp L_2 .

$$I_2 = \dots 0.30 \text{ A} \dots$$

$$V_2 = \dots 1.7 \text{ V} \dots$$

Calculate the resistance R_2 of the filament of lamp L_2 . Use the equation $R_2 = \frac{V_2}{I_2}$.

$$R_2 = \dots\dots\dots$$

The student disconnects the voltmeter. She connects lamp L_3 in series with lamps L_1 and L_2 . She connects the voltmeter across lamp L_3 .

She measures the current I_3 in the circuit and the potential difference V_3 across lamp L_3 .

$$I_3 = \dots 0.26 \text{ A} \dots$$

$$V_3 = \dots 1.2 \text{ V} \dots$$

Calculate the resistance R_3 of the filament of lamp L_3 . Use the equation $R_3 = \frac{V_3}{I_3}$.

$$R_3 = \dots\dots\dots$$

[1 mark]

Question 2c

Calculate $R_1 + R_2 + R_3$. Give your answer to a suitable number of significant figures for this experiment.

$R_1 + R_2 + R_3 = \dots\dots\dots$
[1 mark]

Question 2d

Some students make suggestions about the results of the experiment.

Suggestion **A**: $R_1 + R_2 + R_3$ should be equal to $3 \times R_1$

Suggestion **B**: $R_1 + R_2 + R_3$ should be less than $3 \times R_1$

Suggestion **C**: $R_1 + R_2 + R_3$ should be greater than $3 \times R_1$

State which suggestion **A**, **B** or **C** agrees with your results. Justify your answer by reference to your results.

[2 marks]

Question 2e

Draw a circuit diagram to show the circuit used in part (b) with all three lamps connected in series.

[3 marks]

Question 3a

A student is investigating a circuit containing different lamps.
She is using the circuit shown in Fig. 3.1.

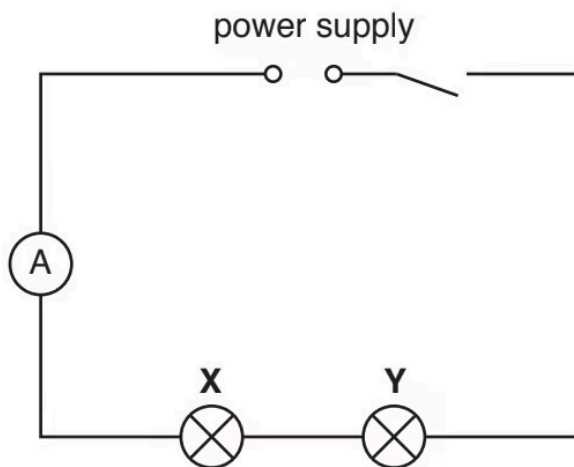



Fig. 3.1

On Fig. 3.1, draw a voltmeter connected so that it measures the potential difference (p.d.) across lamp **X**.

[1 mark]

Question 3b

The student uses the ammeter to measure the current in the circuit.

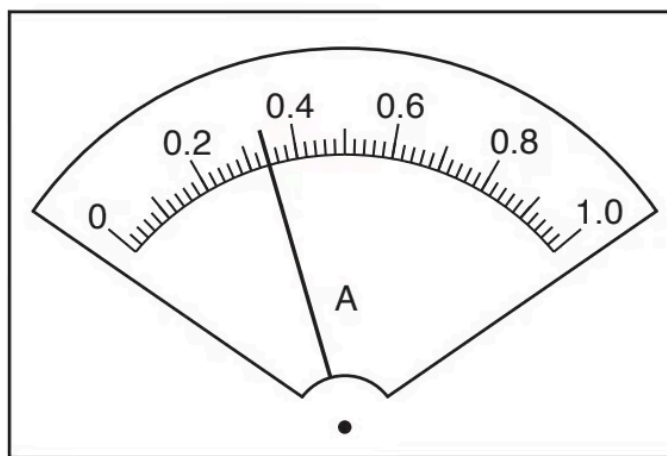**Fig. 3.2**

Record the current I_S in the circuit, as shown in Fig. 3.2.

$I_S = \dots\dots\dots$

[1 mark]

Question 3c

- (i) The student uses the voltmeter to measure the p.d. V_X across lamp **X** and then reconnects the voltmeter to measure the p.d. V_Y across lamp **Y**.

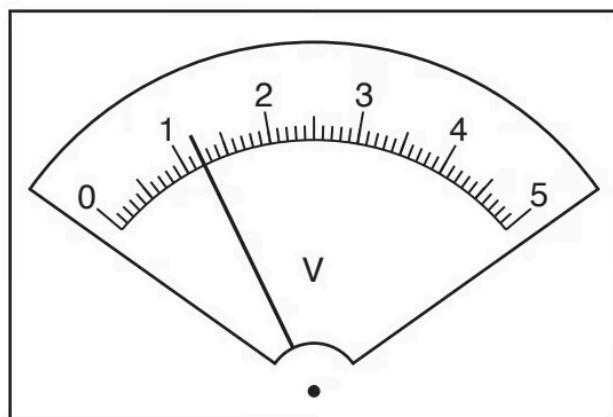


Fig. 3.3

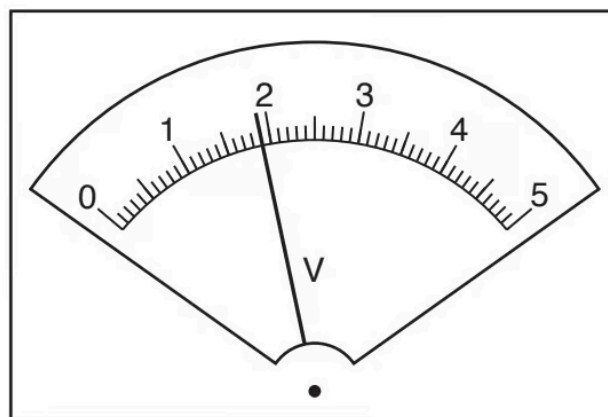


Fig. 3.4

Record the value of the p.d. V_X across lamp **X**, shown in Fig. 3.3.

$V_X = \dots\dots\dots$

Record the value of the p.d. V_Y across lamp **Y**, shown in Fig. 3.4.

$V_Y = \dots\dots\dots$

[1]

- (ii) She then measures the p.d. V_S across both lamps in series.

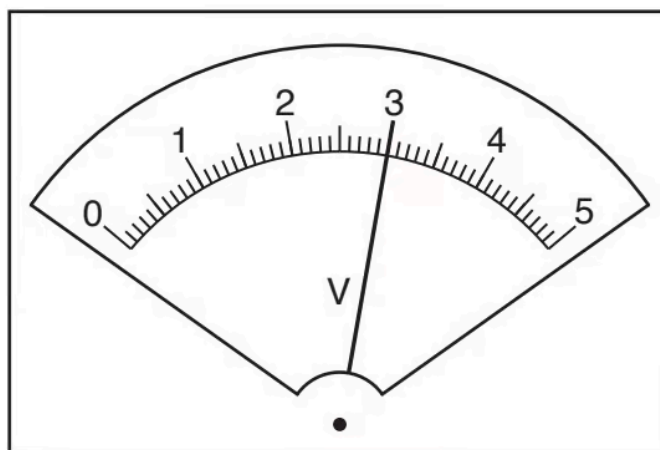


Fig. 3.5

Record the value of the p.d. V_S across both lamps in series, shown in Fig. 3.5.

$V_S = \dots\dots\dots$ [1]

- (iii) A student suggests that V_S should be equal to $(V_X + V_Y)$.

State whether the readings support this suggestion. Justify your statement with reference to the results.

[2]

[4 marks]

Question 3d

Calculate the resistance R_1 of lamp **X**. Use the readings from **(b)** and **(c)(i)** and the equation

$$R_1 = \frac{V_X}{I_S}.$$

$R_1 = \dots\dots\dots \Omega$

[1 mark]

Question 3e**Extended tier only**

- (i) The circuit components are to be rearranged so that
- lamps **X** and **Y** are connected in parallel
 - the ammeter measures the current in lamp **X** only
 - the voltmeter measures the p.d. across the lamps.

Draw a circuit diagram of this arrangement.

[2]

- (ii) The student sets up the circuit as described in **(e)(i)**.

She measures and records the current in lamp **X** and the p.d. across the lamps.

She then calculates a new resistance R_2 for lamp **X** in this parallel circuit.

$$R_2 = 8.3 \, \Omega$$

The student notices that lamp **X** is very bright in this parallel circuit, but it was dim in the series circuit in **(a)**.

Suggest how temperature affects the resistance of a lamp.

Justify your suggestion by reference to the value of R_1 from **(d)** and the value of R_2 .

[2]

[4 marks]